



UTTARAKHAND OPEN UNIVERSITY, HALDWANI (NAINITAL)  
उत्तराखण्ड मुक्त विश्वविद्यालय, हल्द्वानी (नैनीताल)

MCA 1<sup>ST</sup> YEAR 1<sup>ST</sup> SEMESTER ASSIGNMENT

*Last Date of Submission: 15- Jan-2014*

**Course Title: Digital Logic**


**Course Code: MCA-02**

**Year: 2014-2015**

**Maximum Marks: 40 Marks**

Section 'A' contains 08 short answer type questions of 5 marks each. Learners are required to answer 4 questions only. Answers of short answer-type questions must be restricted to 250 words approximately.

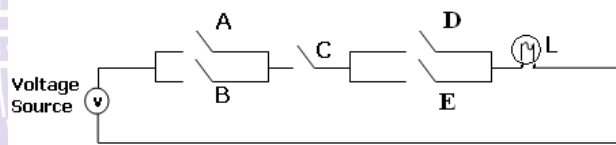1. Express the following switching circuit in binary logic.



2. Perform the following by 2's complement method:  
a)  $10101 - 11011$  b)  $100011 - 1111$
3. Convert the  $(234)_{10}$  into base 8.
4. Multiply  $(34)_8$  by  $(67)_8$
5. Implement the function with NAND gate. a)  $A + B + C$  b)  $ABC + A'B'C' + B$
6. Define combinational logic. Explain the design procedure for combinational circuit
7. What is universal shift register? Draw the circuit diagram of universal shift register and explain its working.
8. Explain the following
  - (i) EPROM
  - (ii) EEPROM

Section 'B' contains 04 long answer-type questions of 10 marks each. Learners are required to answers 02 questions only.

1. What are flip-flops? Draw the state diagram and characteristics equation of T FF, D FF and JK FF?
2. Design and explain the working of a synchronous mod –3 counter
3. Minimize the following function by tabular method:

$$F(w, x, y, z) = \Sigma(0,1,4,5,6,7,9,10,11,14,15)$$

4. Draw the block diagram of a typical (2048 x 16) bits ROM and describes its working principles.

