



Last Date of Submission: 15 May 2016

Course Title: Semiconductor Devices Analog and
Digital electronics

Course Code: PHY-504

Year : 2015-16

Maximum Marks :40

Section A

Section 'A' contains 08 short answer type questions of 5 marks each. Students are required to answer 4 questions only. Answers of short answer type questions should be in 250 words approximately.

- 1- Describe the construction, working, characteristics and applications of LED.
- 2- Explain with the help of neat diagrams, the structure of N-channel FET and its volt ampere characteristics. In what way it is different from a bipolar junction transistor?
- 3- Explain the working of Zener regulated power supply. Explain with an example.
- 4- Explain the concept of feedback with the help of neat diagram. Give the advantage of negative feedback amplifier over positive feedback.
- 5- What are the characteristics of ideal operational amplifier? Explain its different terms.
- 6- By using op amp design a full wave precision rectifier. Explain its working also.
- 7- Draw the circuit diagram of half adder, full adders and subtractor. Explain its working.
- 8- What is a flip flop? Explain clocked RS flip flop and Master Slave JK flip flop.

Section B

Section 'B' contain 04 long answers type question of 10 marks each and students are required to answers 02 questions only.

- 1- Draw the circuit diagram of an operational amplifier as differentiator and integrator. Explain its working.
- 2- State and prove De Morgan's theorems. What are universal building block gates?
- 3- What do you mean by Karnaugh map? How a Boolean function can be simplified with the help of K map. By using example explain it.
- 4- What is multiplexer and demultiplexer? Describe the working of 4 to 1 demultiplexer.